

OUTPUT

 


Figure 1: AND Gate RTL Schematic Block

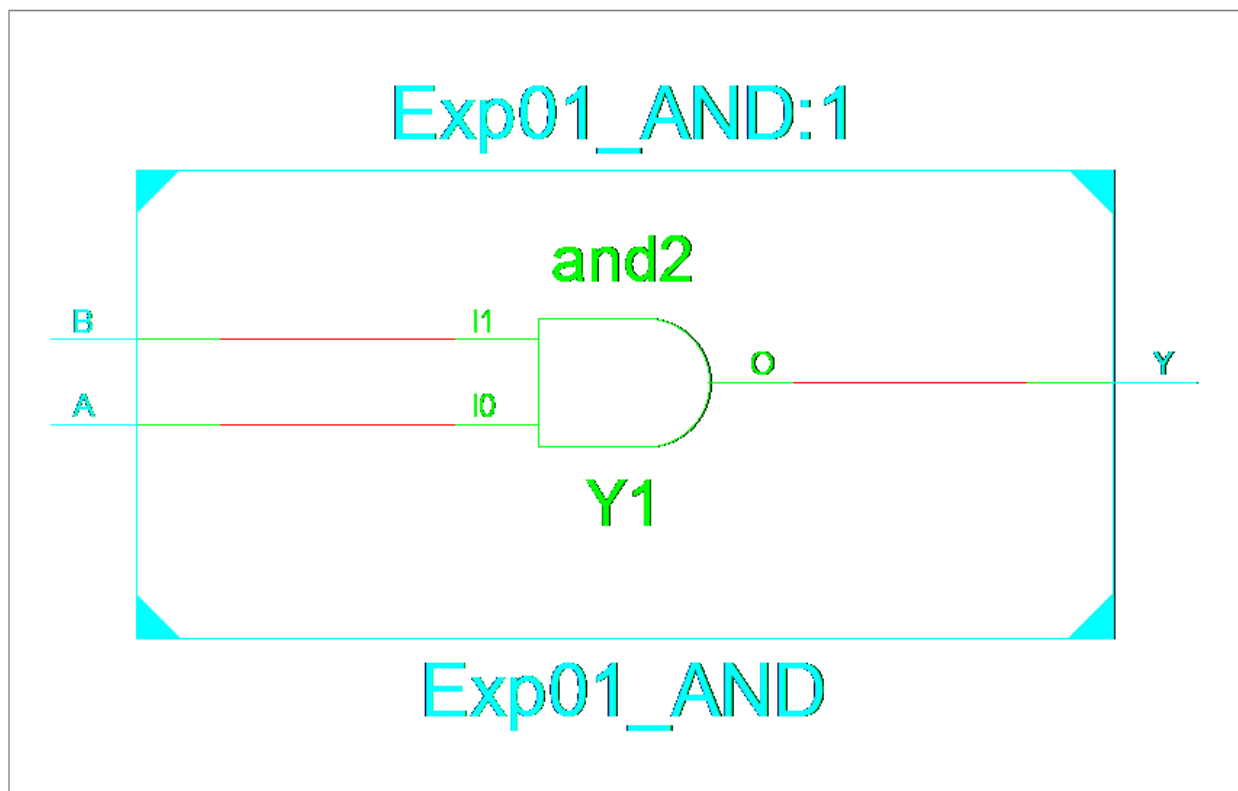


Figure 2: AND Gate RTL Schematic Diagram

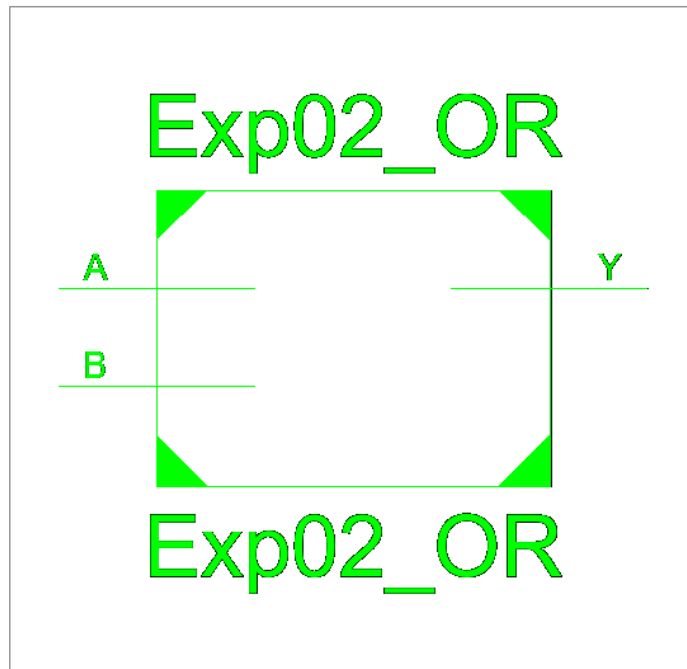


Figure 3: OR Gate RTL Schematic Block


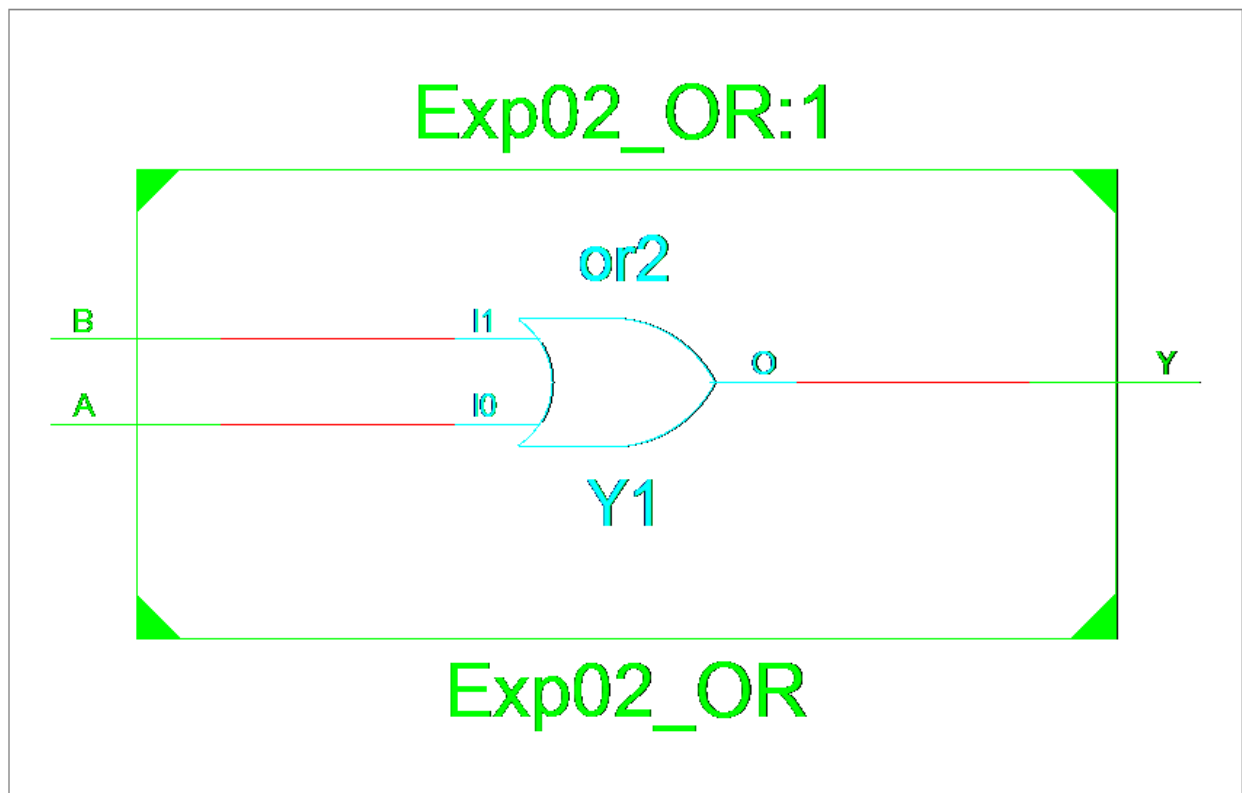


Figure 4: OR Gate RTL Schematic Diagram

Exp03_Function

 

Exp03_Function

Figure 5: $AB + C$ RTL Schematic Block

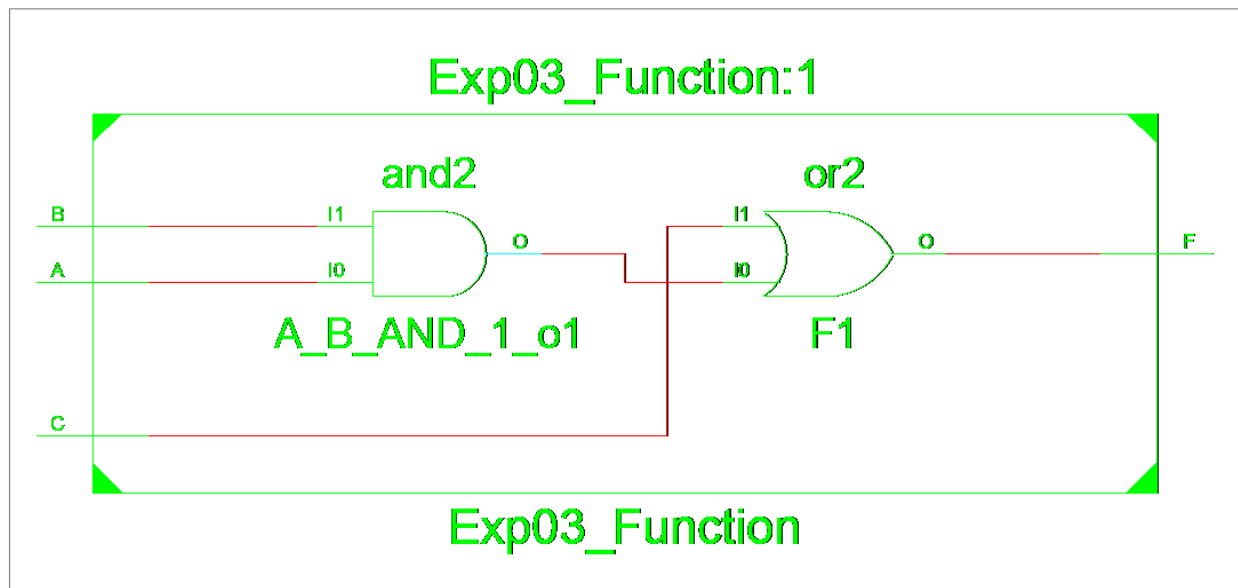


Figure 6: $F = AB + C$ RTL Schematic Diagram

 


Figure 7: Test Bench of AND Gate

 


Figure 8: Test Bench of OR Gate

 


Figure 9: Test Bench of $F = AB + C$