

OUTPUT



Figure 1: 4 Bit Adder Schematic Block


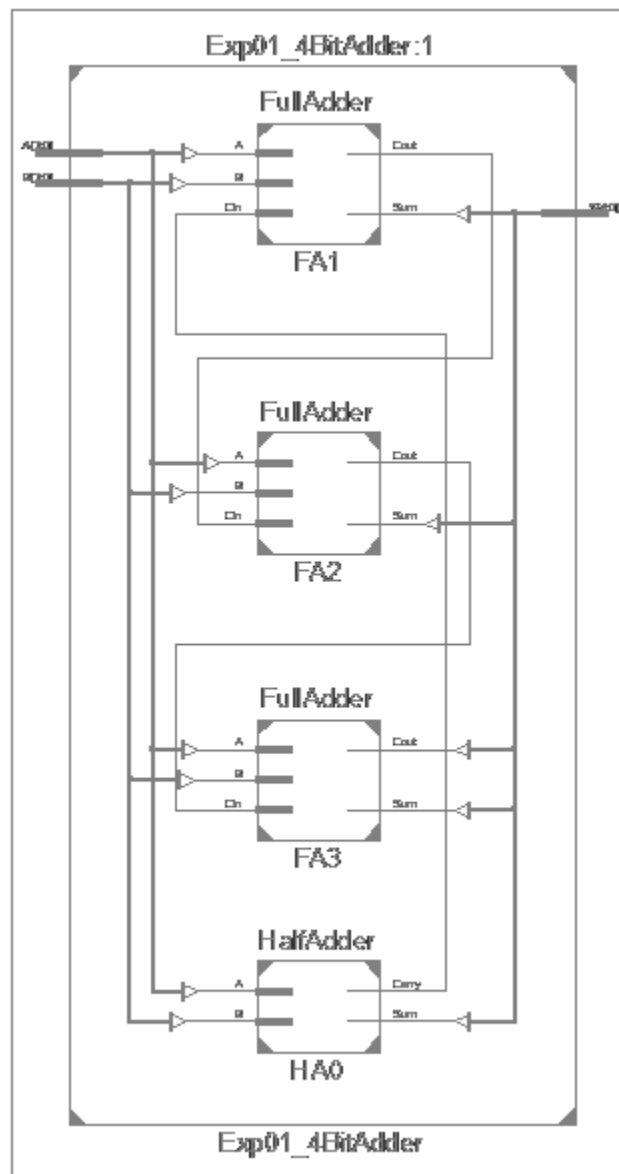


Figure 2: 4 Bit Adder RTL Schematic Diagram

Exp02_2BitMultiplier

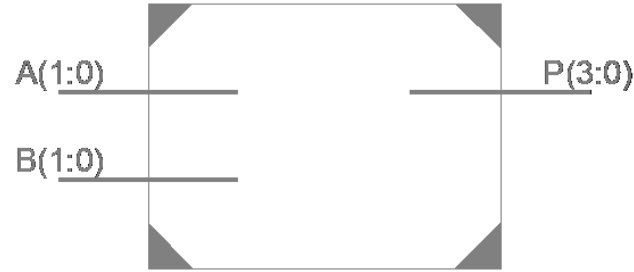

Exp02_2BitMultiplier

Figure 3: 2 Bit Multiplier RTL Schematic Block

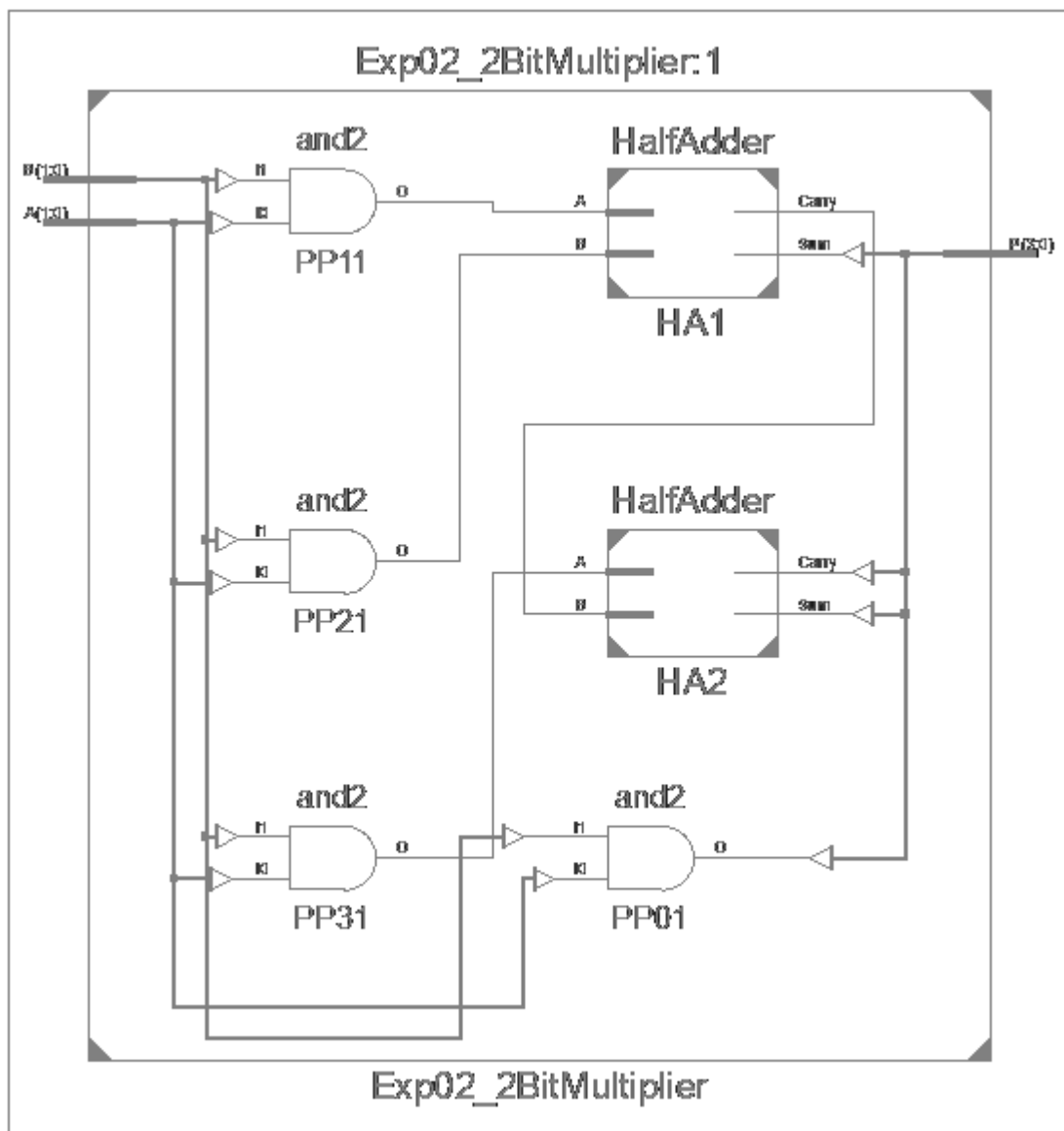


Figure 4: 2 Bit Multiplier RTL Schematic Diagram

Exp03_SimpleProcessor

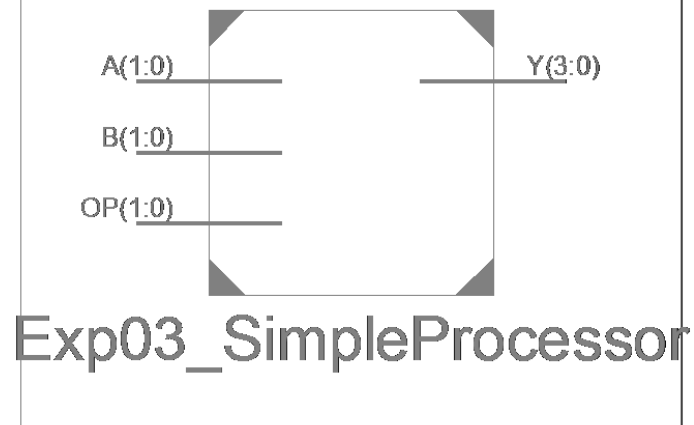


Figure 5: Simple Processor Block

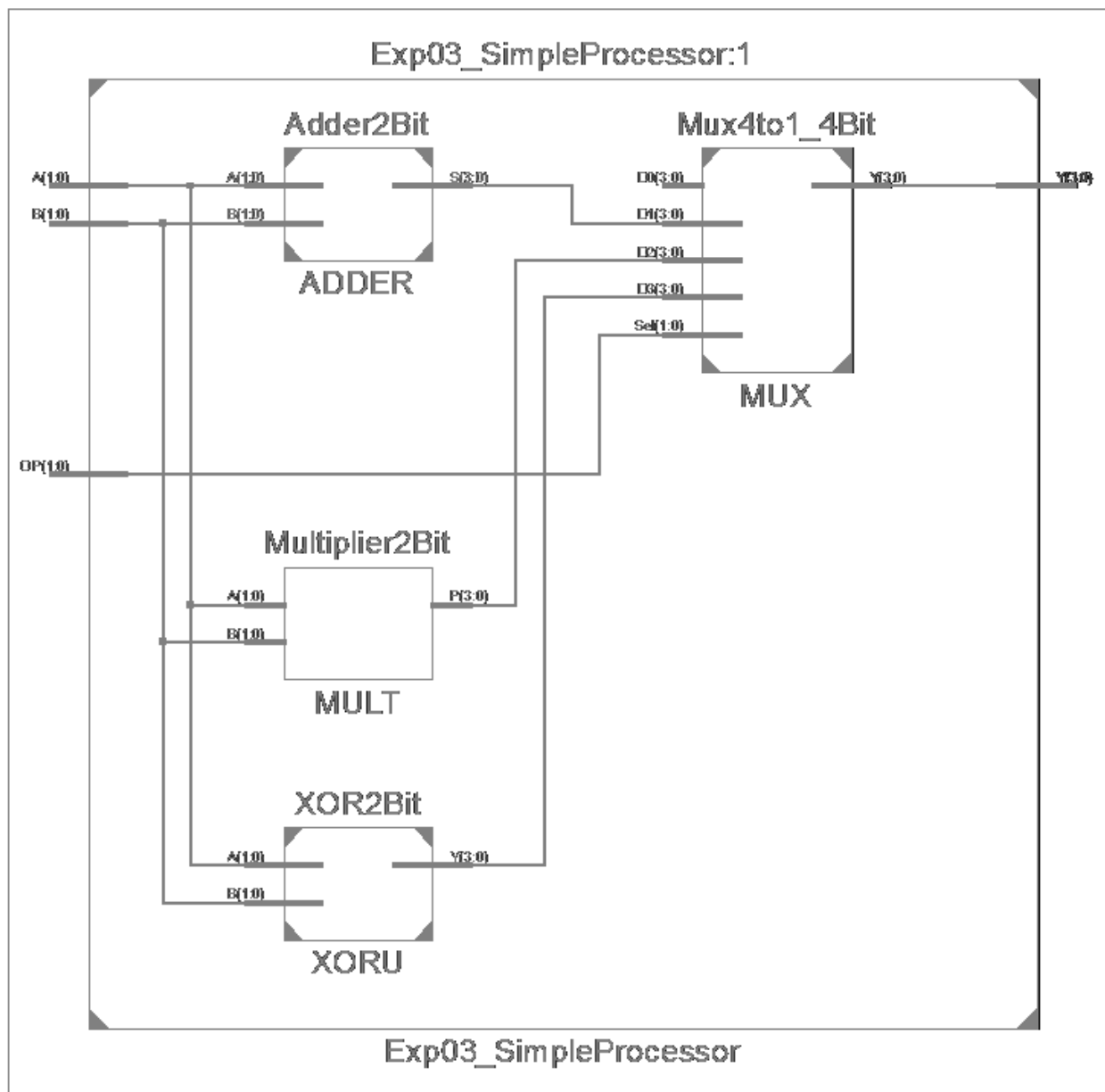


Figure 6: Simple Processor RTL Schematic Diagram